

Resistance and Current

Tuesday, November 28, 2023 1:02 PM

Current in an object depends on how resistive a material is to charge passing thru it.

Objects that have little resistance are called good conductors, **metal** and certain carbon samples are good conductors. Current is high in **good conductors**.

Objects that have large resistance are called **insulators**. Materials include plastics, rubber, and typical **non-metal compounds**. These have covalent bonds.

Resistance is the measure of how hard it is to move charge through a material. Metals have low resistance, non-metals have high resistance. Units are Ohms.

R in formulas


ohms (Ω)

When resistors are connected one after the other we call this series:

$$R_{series} = R_1 + R_2 + R_3 \dots$$




Find the total resistance in series:

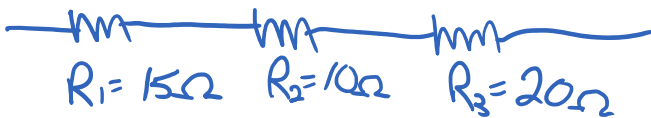

$$\begin{aligned} R_{series} &= R_1 + R_2 + R_3 \\ &= 15 + 10 + 20 \\ &= 45 \Omega \end{aligned}$$

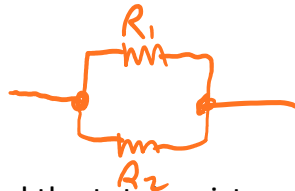
When resistors provide 2 routes between the same points we call this parallel. In parallel total resistance DROPS



It's weird!

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

Find the total resistance in parallel:

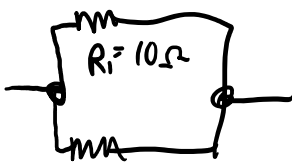

$$R_2 = 20 \Omega$$


$$6 \Omega$$



$$\frac{1}{R_p} = \frac{1}{10} + \frac{1}{20} = 0.15 \leftarrow \text{That is } \frac{1}{R_p}$$

$$R_p = (0.15)^{-1} = 6.67 \Omega$$

less than the 10!

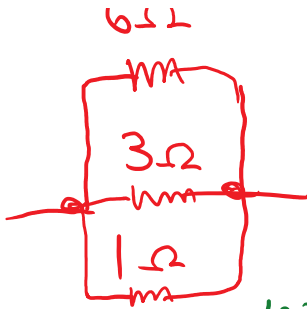


$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3} + \frac{1}{1} = 1.5 \leftarrow \frac{1}{R_p}$$

less than the 10!

$$R_p = (1.5)^{-1} = 0.67 \Omega$$


less than 1Ω

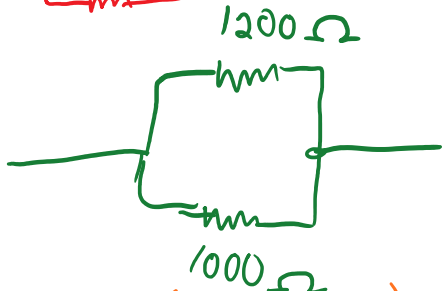

$$\frac{1}{R_p} = \frac{1}{1200} + \frac{1}{1000} = 1.83 \times 10^{-3}$$

$$R_p = (1.83 \times 10^{-3})^{-1} = 545 \Omega$$


Mix and match resistances

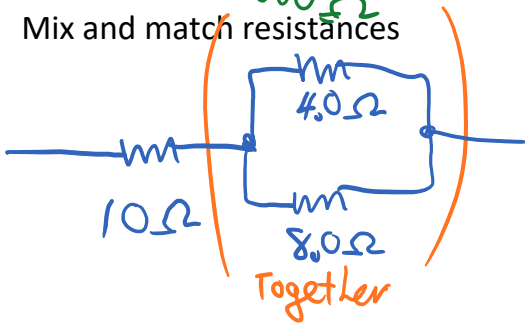

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{8} = 0.375 \quad R_p = 2.67 \Omega$$

then the 2.67 is series with 10
so


$$10 + 2.67 = 12.7 \Omega$$

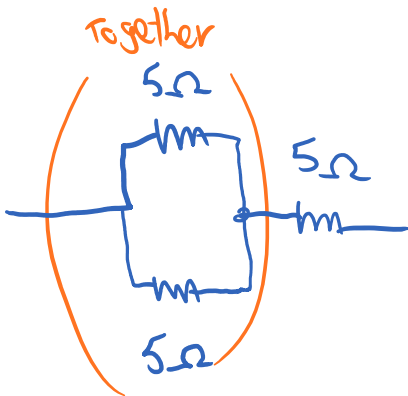

$$R_p = \frac{1}{\frac{1}{5} + \frac{1}{5}} = \frac{2.5}{1} = 2.5 \Omega$$

then series

$$2.5 + 5 = 7.5 \Omega$$

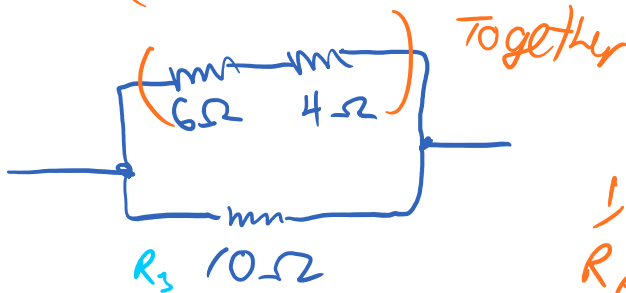


$$R_s = 6 + 4 = 10 \leftarrow$$


now

$$\frac{1}{R_p} = \frac{1}{R_3} + \frac{1}{R_s}$$
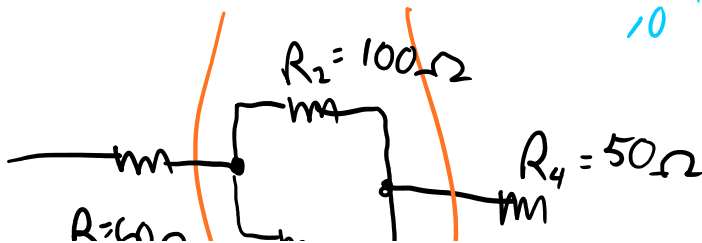
$$= \frac{1}{10} + \frac{1}{10} = \frac{2}{10} \Rightarrow \frac{10}{2} = 5.0 \Omega$$


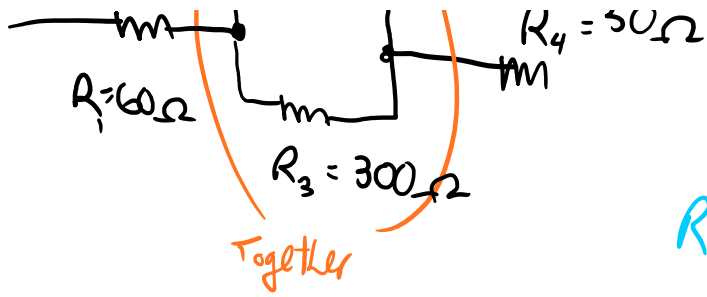
$$\frac{1}{R_p} = \frac{1}{100} + \frac{1}{50} = \frac{4}{100} \Rightarrow \frac{100}{4} = 25 \Omega$$



$$\frac{1}{R_p} = \frac{1}{100} + \frac{1}{300} = \frac{4}{300} \Rightarrow 75\ \Omega$$

$$R_s = 60 + 75 + 50 = 185\ \Omega$$

Current is caused to flow by a voltage difference between 2 points in a conductor. The current is slowed or reduced by the resistance between the points.

$I = \Delta V / R$ this is called Ohm's Law

A cat is connected to a household supply and draws 0.480 A, find the resistance of the cat.

Find the current in 12W lightbulb connected to a household supply, use that to find the resistance of the bulb.

A 10 W bulb is connected in series to a 5.0 W bulb and a 6.0 V supply, find the current. Find the total power.

A 6.0 V supply is 10 W bulb and connected in parallel to a 5.0 W bulb. Find the current. Find the total power.

300 W are used to power the circuit at the right, find the current flowing from the source.