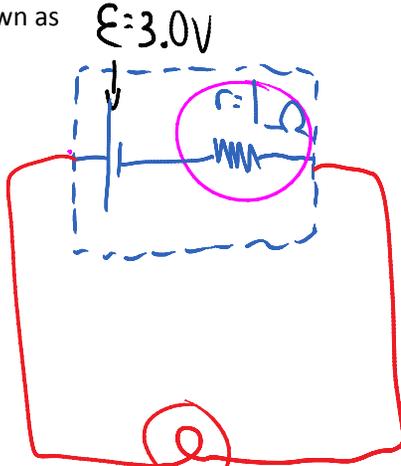


Terminal Voltage and Charging cells

Thursday, April 08, 2010
8:02 PM

All cells have an internal resistance to current flow. We call this the INTERNAL RESISTANCE. A cell is then drawn as

ends of cell



caused by chemistry in cells

\mathcal{E} = source voltage
= EMF

$$\mathcal{E} = I r + V_T$$

Total CURRENT


$$\mathcal{E} - I r = V_T$$

$R_i = 8 \Omega$

① Find $I_{TOT} = \frac{\mathcal{E}}{R_{TOT}} = \frac{3}{9} = 0.33 A$

$V_T = 3 - (.33)(8) = 2.69V$

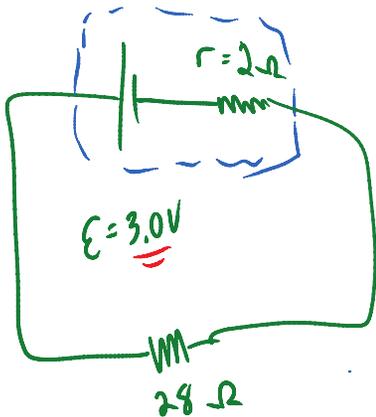② find terminal voltage $V_T = \mathcal{E} - I r$




What is the V_T ?

① $I_{TOT} = \frac{\mathcal{E}}{R_{TOT}} = \frac{3}{30} = 0.10 A$

② $\mathcal{E} - I r = V_T = 3 - (.10)(2) = 2.67V$

$\mathcal{E} = V_T$ when $I = 0$ ← cell not in use

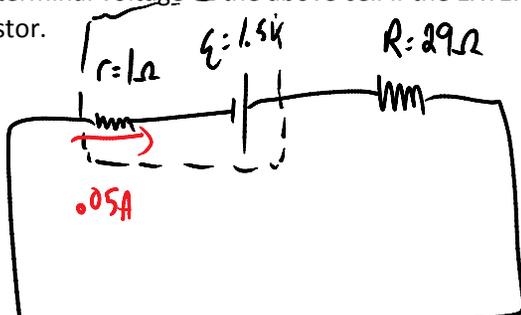Recalculate the terminal voltage of the above cell if the EXTERNAL resistor is replaced with a 29Ω resistor.



$$I_0 = \frac{\mathcal{E}}{R_{TOT}} = 1.5 A$$




$$K_{TOT} = \frac{1.5}{30} = .05A$$

$$V = I r = (.05)(1) = .05V$$

$$V_T = \mathcal{E} - I r = 1.5 - .05 = 1.45V$$

What I would allow $V_T = \mathcal{E} ?!!$

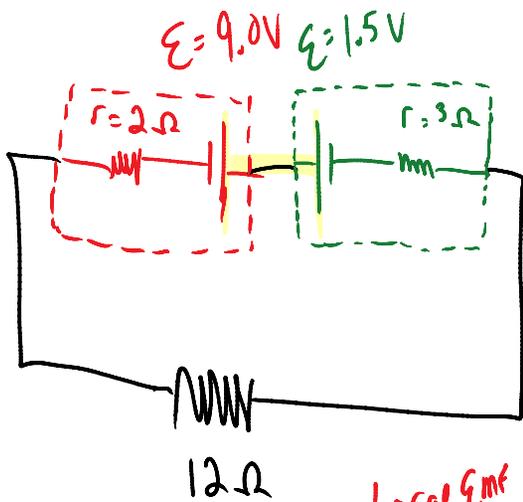Charging Cells: this is done by reversing the chemical reactions in the cell. Only certain cells may be recharged. In order to reverse the chemical reactions the current through the cell must be driven backwards from the usual direction. How could this be accomplished?



Connect the cell to be recharged backward to a larger EMF

Find V_T for each cell

$$I_{TOT} = \frac{\mathcal{E}_{TOT}}{R_{TOT}} = \frac{9 - 1.5}{17} = 0.44A$$

Large EMF is same

$$V_T = \mathcal{E} - I r = 9 - .44(2) = 8.12V$$


$$V_T = \mathcal{E} - I r = 1.5 + (.44)(3) = 2.8V$$

← 9V EMF

small emf
 $I = -I$ means $\mathcal{E} + I r = V_T$
 ← discharging
 $V_T = \mathcal{E} + I r$
 ← recharging

Example: A 9.0 V transformer is used to charge a 1.5 V cell. If the cell has internal resistance 2 Ω and the transformer has internal resistance 1 Ω

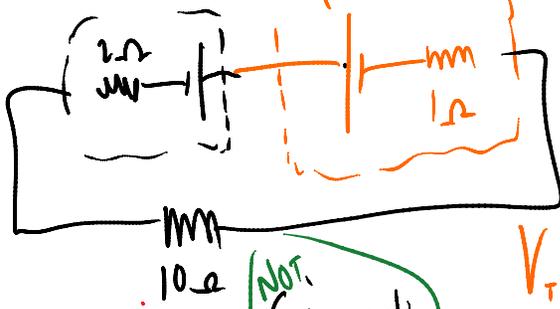Example: A 9.0 V transformer is used to charge a 1.5 V cell. If the cell has internal resistance 2.0 Ω and the transformer has internal resistance 1.0 Ω, what current flows through the cell and what is the terminal voltage of the cell and transformer. There is a 10 Ω resistor in the circuit.



$$I_{TOT} = \frac{\mathcal{E}_{TOT}}{R_{TOT}} = \frac{7.5}{13} = .58 A$$

$$V_T = 9 - .58(1) = 8.42 V$$

$$V_T = 1.5 - (-.58) \left(\frac{2}{1.5 + 1.16} \right) = 2.65 V$$

Booklet completed
 Text stuff done
 #5 and 6 page 192 as well as
 2, 3, 7, 8, 11 - 16, 19, 21 - 24, 25 page 197


NOT Giancoli!
 Ch 6

Charging cells changes the terminal voltage equation. $\mathcal{E} - (I)r = V_T$
 Because current is a vector, and reversing a vector's direction is symbolized by making it negative, the terminal voltage formula for a charging cell is:



$\mathcal{E} - (-I)r = V_T$ or $\mathcal{E} + Ir = V_T$ (charging)

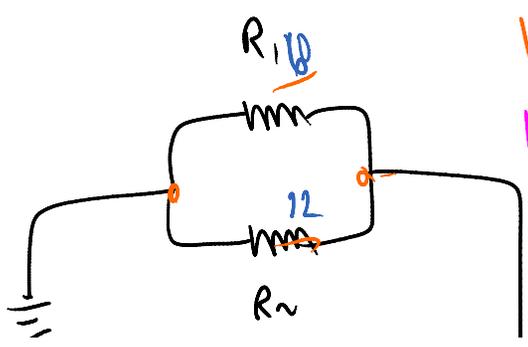
A 1.5 V cell with internal resistance 1.0 Ω is charged by a 3.0 V battery with internal resistance 2.0 Ω. If the circuit has an additional 10 Ω resistor draw the circuit and find the terminal voltage of each cell.



$$V_1 = V_2$$

$$\frac{1.60}{12} = \frac{1.2}{12}$$

$$I_1 = 5 I_2$$

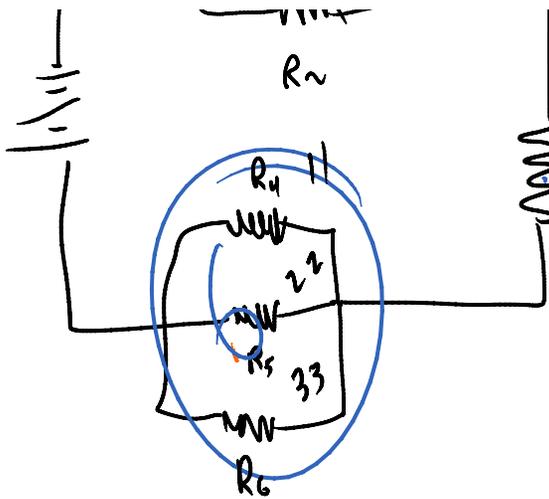

$$I_1 = 5 I_2$$


$$5 I_2 + I_2 = 6A$$

$$\frac{6}{66} + \frac{3}{33} + \frac{2}{33} = \frac{11}{66}$$

$$R_p = \frac{66}{11} = 6$$

Garden
Ohm

10

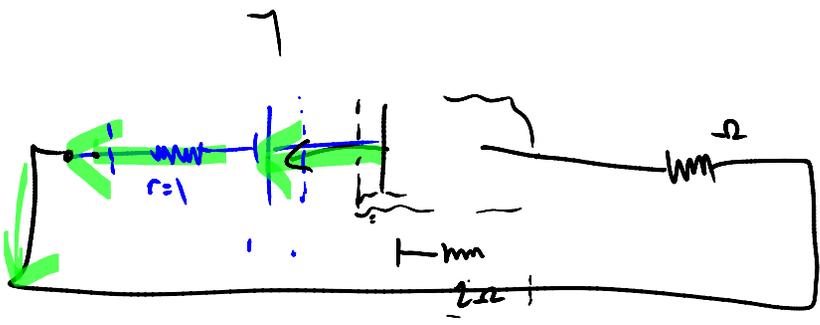

$$V_0 = 3 - 1.5 = 1.5V$$

$$R_0 = 13 \Omega$$

$$I_0 = \frac{V_0}{R_0} = \frac{1.5}{13} = 0.115 A$$

Voltage outside



V_0
 $R_0 = 13 \Omega$

$R_0 = 13$

R_1 ← Voltage outside cell used in circuit

$\mathcal{E} - I_r = V_T$
 $3 - (.115)(13) = 2.77 V$

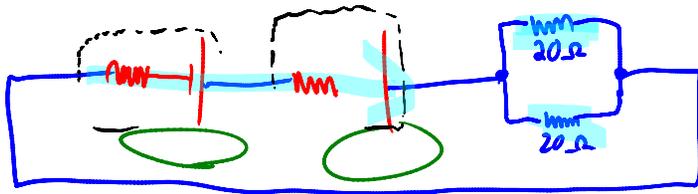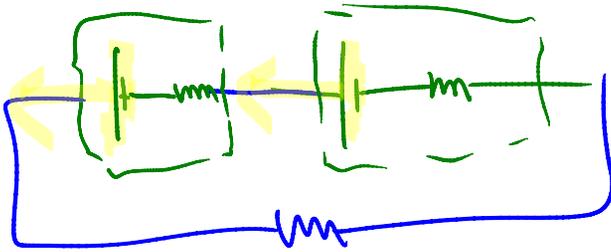
$\mathcal{E} - I_r = V_T$
 $1.5 - (-.115)1 = V_T = 1.62 V$



$\frac{\mathcal{E}_1 + \mathcal{E}_2}{R_{tot}} = \frac{3}{R_{tot}}$

$\mathcal{E} = 0.26$
 $R_0 = 11.6$
 $.28 R_1 = .8$
 $.26 R_2 = .8$
 $R_3 = 20$
 $.129 R_4 = 20$

Finish Booklet

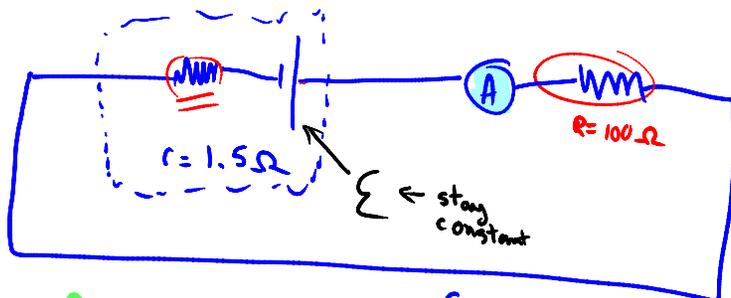

Use this

$\mathcal{E} = I R_{tot}$
 A reads 12 mA, find the terminal voltage
 charging find V_T of the external resistor

$\mathcal{E} = I_{TOT} R_{TOT}$
 $(.012)(101.5) = 1.218V$


A reads 12 mA, find the terminal voltage
 charging find V_T if the external resistor is replaced with 50 Ω resistor
 explain why V_T increased/decreased

$V_T = \mathcal{E} - I r$
 $1.218 - (.012)(1.5) = 1.20V$

$V_T = \mathcal{E} - I r$
 $1.218 - (.023)(1.5) = 1.18V$

$\mathcal{E} = I_{TOT} R_{TOT}$
 $1.218 = I_{TOT} 51.5$
 $I_{TOT} = 0.023 A$

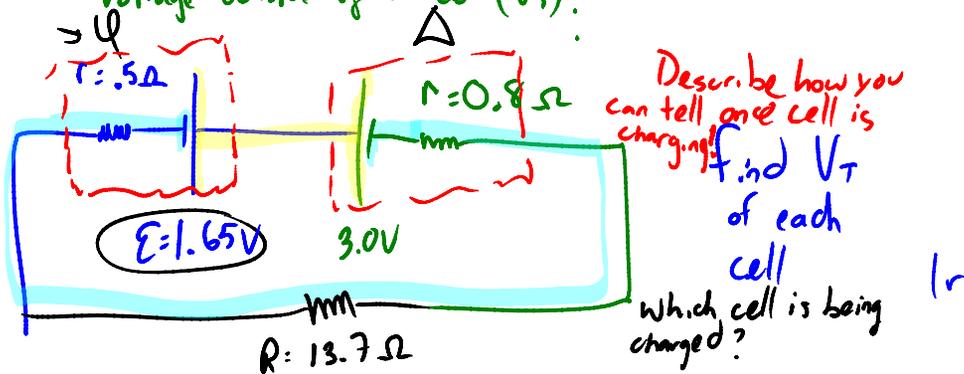B/c I_{TOT} increases the voltage consumed in cell's internal resistance ($I r$) increased. Resulting in less available voltage outside of the cell (V_T).



Cell's connected + to +
 charging - to -

$V_T = \sum_{all\ cells} \pm I r$

$V_T = 1.65 + I (.5)$

$1.65 + (.09)(.5) = 1.7V$

$I_{TOT} = \frac{V_{TOT}}{R_{TOT}}$
 $= \frac{3 - 1.65}{15}$
 $= \frac{1.35}{15} = .09 A$

$V_T = \mathcal{E} - I r$
 $= 3 - (.09)(.8) = 2.93V$

∇ is being charged, Δ is discharging

1-3, 5, 7, 8, 10-16,
 18-22, 24,
 25 P. 197
 26



$I_0 = 115 \downarrow$
 $R_0 = 13 \Omega \uparrow$
 $r_1 = 1$
 $r_2 =$
 $r_3 =$

1
 10
 2

10 \uparrow
 2

10 Ω
 R_v

$\mathcal{E}_1 - \mathcal{E}_2 = 1.5$

R_v

$\mathcal{E}_1 - \mathcal{E}_2 = 1.5$ Black cell
 V_1
 V_2
 V_3

2

Red cell $\mathcal{E} - Ir = V_T$
 $3 - (0.115)(2) = V_T = 2.77V$
 $1.5 - (-0.115)(1)$

$\mathcal{E} = Ir = V_T =$



$= 1.62V$

← current decrease if $R \uparrow$
increase if $R \downarrow$

How does changing the external resistor affect the a) current flow

b) terminal voltage of large cell

c) terminal voltage of charging cell

increase if $R \uparrow$
decrease if $R \downarrow$

decrease if $R \uparrow$
increase if $R \downarrow$

Do 4-6 p. 192
1-3 p. 191